

**University of Nevada, Las Vegas**  
**Department of Electrical and Computer Engineering**

**CPE 302 - Synthesis and Verification Using Programmable Devices**

**Final Project Report**  
**Color Match RNG Game**

**Yanai Avila**  
**Spring 2023**


## 1. Introduction

**Board Used:** Altera DE2 Cyclone II ([board overview](#))

**Language:** VHSIC Hardware Description Language (VHDL)

**Project Description:** For my final project, I implemented a simple mini-game that uses a random number generator. The player chooses a sequence of 4 colors they think will be randomly generated. They input this guess using the switches on the DE2 board. 00, 01, and 10. The 4 colors are randomly generated and displayed on the 7-segment displays. For each color the player guesses correctly, they gain a point.


RTL View

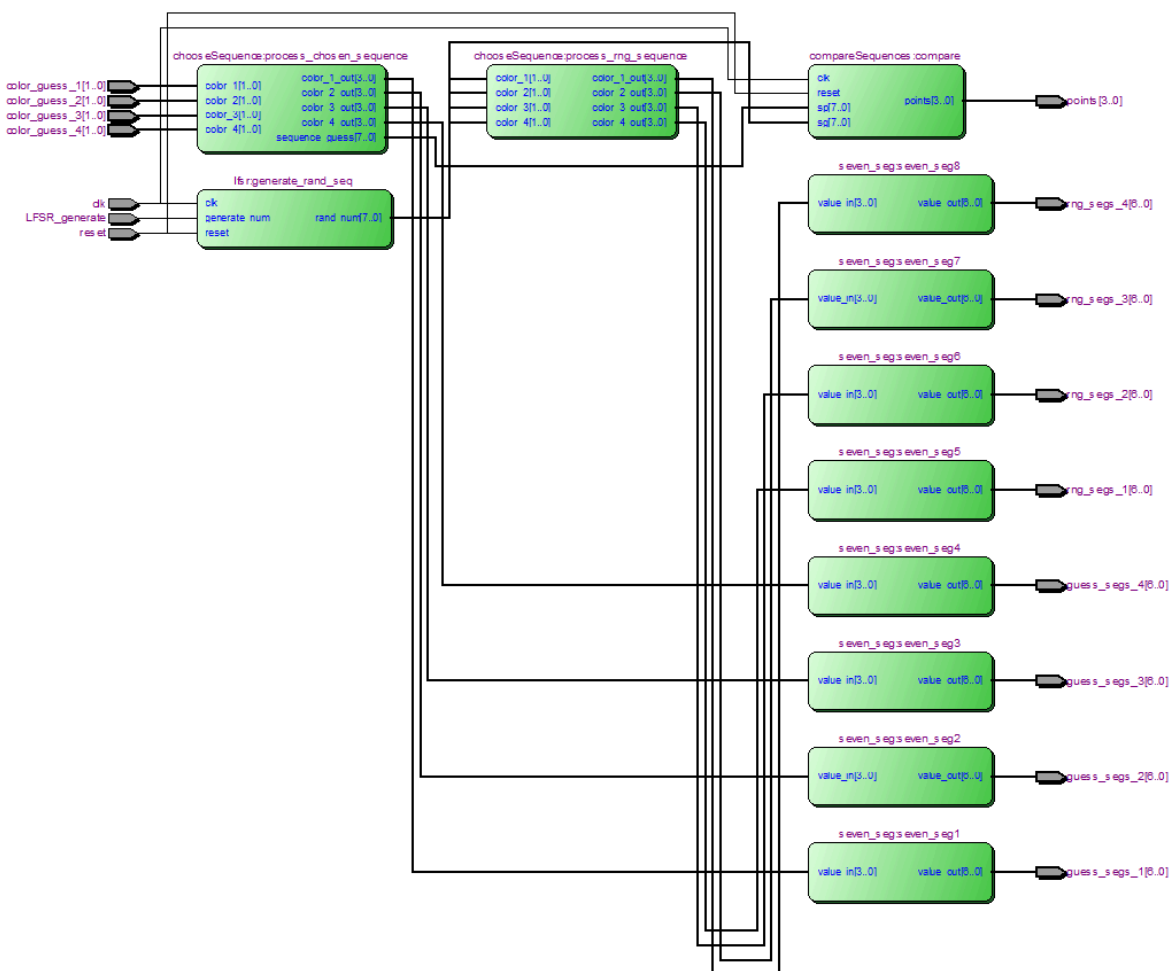

**Note:** Modules are explained in section 2.
 
## 2. Modules

**LFSR( )** - The main component of my project is a Linear Feedback Shift Register (LFSR). An LFSR is a pseudo-random number generator, and in my project, an LFSR is used to generate a random 8-bit number. This 8-bit output is used in another module to determine how many points the player gains based on how it compares to the 8-bit number that the player inputs as their guess. The figure below shows how XORing the tap bits for an n-bit number can generate a wide range of bit combinations. The LFSR will keep cycling through these combinations until a generate signal goes high. In my module, the generate\_num signal has to go high for the rand\_num output variable to take in the random combination at that point.



# of Bits	Length of Loop	Taps
2	3 *	[0,1]
3	7 *	[0,2]
4	15	[0,3]
5	31 *	[1,4]
6	63	[0,5]
7	127 *	[0,6]
8	255	[1,2,3,7]
9	511	[3,8]
10	1,023	[2,9]
11	2,047	[1,10]
12	4,095	[0,3,5,11]
13	8,191 *	[0,2,3,12]
14	16,383	[0,2,4,13]
15	32,767	[0,14]
16	65,535	[1,2,4,15]
17	131,071 *	[2,16]
18	262,143	[6,17]
19	524,287 *	[0,1,4,18]
20	1,048,575	[2,19]
21	2,097,151	[1,20]
22	4,194,303	[0,21]
23	8,388,607	[4,22]
24	16,777,215	[0,2,3,23]
25	33,554,431	[2,24]
26	67,108,863	[0,1,5,25]
27	134,217,727	[0,1,4,26]
28	268,435,455	[2,27]
29	536,870,911	[1,28]
30	1,073,741,823	[0,3,5,29]
31	2,147,483,647 *	[2,30]
32	4,294,967,295	[1,5,6,31]

\* I used tap bits 1, 2, 3, 7


## Code for LFSR

```

180 entity lfsr is
181   Port ( clk      : in  std_logic;
182         reset     : in  std_logic;
183         generate_num : in  std_logic;
184         rand_num    : out std_logic_vector(7 downto 0));
185 end lfsr;
186
187 architecture behavioral of lfsr is
188   signal current_combo, next_combo: std_logic_vector(7 downto 0);
189   signal feedback: std_logic;
190 begin
191   update: process (clk,reset)
192   begin
193     if (reset = '1') then
194       current_combo <= (0 => '1', others => '0'); -- if reset, 00000001(cant be 0)
195       -- at rising clk edge
196     elsif (clk = '1' and clk'event) then
197       current_combo <= next_combo;
198     end if;
199   end process;
200
201   -- The feedback bit will be the XORing of differnt bits
202   feedback <= current_combo(4) xor current_combo(3) xor current_combo(2) xor current_combo(0);
203   -- shift current cobinatrion to the right and make the feedback bit the first bit
204   next_combo <= feedback & current_combo(7 downto 1);
205
206   -- When the pushbutton is pressed
207   generat: process(generate_num)
208   begin
209     if(generate_num = '1') then
210       -- the random number will take the value of the current combo(constantly changing)
211       rand_num <= current_combo;
212     end if;
213   end process generat;
214 end behavioral;

```

## Simulation for LFSR

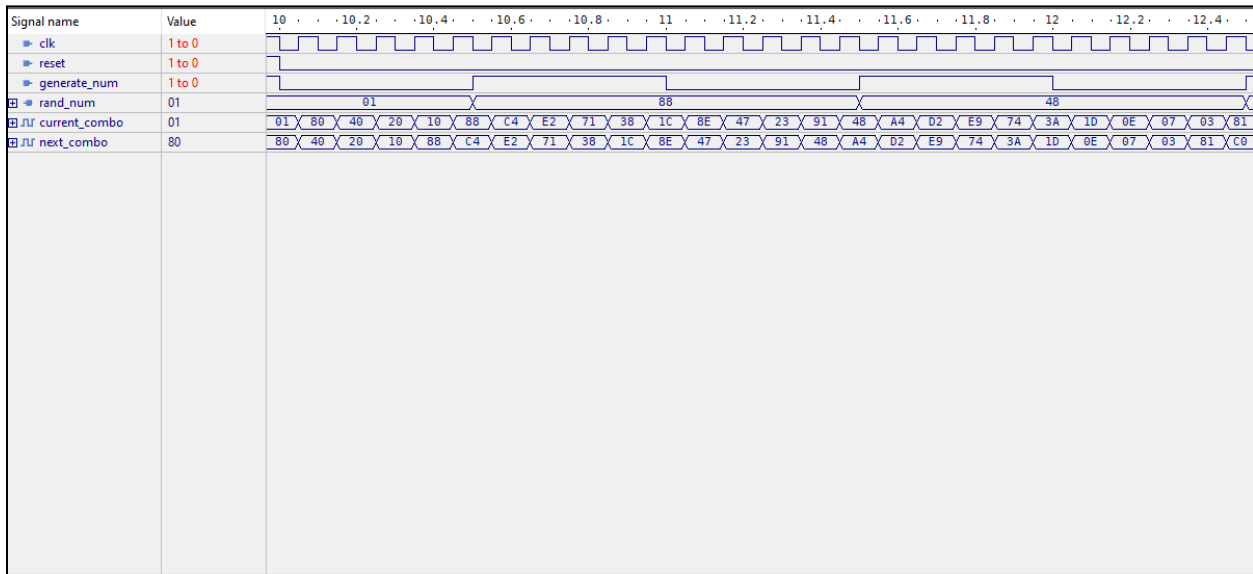

**NOTE:** Every time generate\_num goes high, the rand\_num (which is the output of the module) takes the value of current\_combo. Current\_combo changes rapidly at each clock edge, and when the player presses the generate pushbutton, the random number at that clock edge is displayed to the designated 7-segment display for the generated color sequence.

**chooseSequence( )** - This module is a lookup table that processes *both* the number that the player inputs using the input switches and the random number generated using the LFSR. This allows the user to input their guess using the designated input switches and see their 4 selected colors on the 7-segment displays as well as see the random 4 colors on some other 7-segment displays. Even though the module is called “choose” sequence, it is also used for the generated number since the processing is the same for both.

This module takes in the 8-bit guess or 8-bit generated number, and processes it to be compatible with the input needed input for the 7-segment display module. This 8 bit input is divided into 2-bit signals for each 7-segment display, so in total there are 4 different combinations (00, 01, 10, 11), each representing a different color. These combinations are as follows:

- 00 is blue → “8/B” on the 7-segment display
- 01 is green G → “6/G” on the 7-segment display
- 10 is purple P → “P” on the 7-segment display
- 11 is yellow Y → “y” on the 7-segment display



Here we see that 00 is blue, so the output of this sequence is 0000, and this will be the input for the 7-segment display module which outputs the letter B (looks like “8”) on the 7-segment display. The same applies to 01, which will output 0001 (corresponds to green), 10, which will output 0010 (corresponds to purple), and 11, which will output 0011 (corresponds to yellow).

**Note:** I could have left the signals to be 2 bits, but I made the input signal for the 7-segment display module to be 4 bits to be able to accommodate more labels/colors for future improvements or additions to the game.

Code segment for the processing of color 1 (guess or generated)

```
-- case for color guessed 1
case(color_1) is
  when "00" => color_1_out <= "0000"; --B (8)
  when "01" => color_1_out <= "0001"; --G
  when "10" => color_1_out <= "0010"; --P
  when "11" => color_1_out <= "0011"; --Y
  when others => color_1_out <= "1111";
end case;
```

Finally, this module combines all these outputs into a sequence\_guess variable by concatenating the 2 bit numbers together into an 8 bit number for easier use. This output is used in the compare sequences module to determine how many points the players gain. Again, this is also used for the generated number.

**seven\_seg()** - This decoder is used to take a 4-bit value and convert it to a 7-bit signal to be able to display information on the 7-segment displays. The input is taken from the chooseSequence() module and the output is mapped to the displays (see chooseSequence() for mapping details)

```

324 library ieee;
325 use ieee.std_logic_1164.all;
326 entity seven_seg is
327     port(
328         value_in : in std_logic_vector(3 downto 0);
329         value_out : out std_logic_vector(6 downto 0)
330     );
331 end seven_seg;
332
333 architecture behavior of seven_seg is
334 begin
335     process(value_in)
336     begin
337         case(value_in) is
338             when "0000" => value_out <= "0000000"; --B
339             when "0001" => value_out <= "0000010"; --G
340             when "0010" => value_out <= "0001100"; --P
341             when "0011" => value_out <= "0010001"; --Y
342             when "0100" => value_out <= "0011001"; --4
343             when "0101" => value_out <= "0010010"; --5
344             when "0110" => value_out <= "0000010"; --6
345             when "0111" => value_out <= "1111000"; --7
346             when "1000" => value_out <= "0000000"; --8
347             when "1001" => value_out <= "0010000"; --9
348             when "1010" => value_out <= "0001000"; --a
349             when "1011" => value_out <= "0000011"; --b
350             when "1100" => value_out <= "1000110"; --c
351             when "1101" => value_out <= "0100001"; --d
352             when "1110" => value_out <= "0000110"; --e
353             when others => value_out <= "0001110";
354         end case;
355     end process;
356 end behavior;

```

**compareSequences()** - This module compares the sequence that was randomly generated to the sequence that the player guessed. The number of points is outputted to 4 LEDs on the board. The number of points depends on how many colors match. If the player gains 1 point, 1 LED lights up. If 2 points, 2 LEDs light up, and so on.


```

245 architecture Behavioral of compareSequences is
246     signal p0, p1, p2, p3: std_logic;
247 begin
248     process(clk, sg)
249     begin
250         if(sp(7 downto 6) = sg(7 downto 6)) then
251             p0 <= '1';
252         else
253             p0 <= '0';
254         end if;
255
256         if(sp(5 downto 4) = sg(5 downto 4)) then
257             p1 <= '1';
258         else
259             p1 <= '0';
260         end if;
261
262         if(sp(3 downto 2) = sg(3 downto 2)) then
263             p2 <= '1';
264         else
265             p2 <= '0';
266         end if;
267
268         if((sp(1 downto 0) = sg(1 downto 0))) then
269             p3 <= '1';
270         else
271             p3 <= '0';
272         end if;
273     end process;
274
275     points <= p0 & p1 & p2 & p3;
276 end Behavioral;

```

### 3. Pin Assignments

Pin assignments on board

 



## Pin assignments on Active-HDL

Node Name	Direction	Location	I/O Bank	VREF Group	Fitter Location	I/O Standard	Reserved	Current
in [clk]	Input	PIN_N2	2	B2_N1	PIN_N2	3.3-V LV..default		24mA
color_guess_1[1]	Input	PIN_AE14	7	B7_N1	PIN_AE14	3.3-V LV..default		24mA
color_guess_1[0]	Input	PIN_P25	6	B6_N0	PIN_P25	3.3-V LV..default		24mA
color_guess_2[1]	Input	PIN_AD13	8	B8_N0	PIN_AD13	3.3-V LV..default		24mA
color_guess_2[0]	Input	PIN_AF14	7	B7_N1	PIN_AF14	3.3-V LV..default		24mA
color_guess_3[1]	Input	PIN_C13	3	B3_N0	PIN_C13	3.3-V LV..default		24mA
color_guess_3[0]	Input	PIN_AC13	8	B8_N0	PIN_AC13	3.3-V LV..default		24mA
color_guess_4[1]	Input	PIN_A13	4	B4_N1	PIN_A13	3.3-V LV..default		24mA
color_guess_4[0]	Input	PIN_B13	4	B4_N1	PIN_B13	3.3-V LV..default		24mA
guess_segs_1[6]	Output	PIN_V13	8	B8_N0	PIN_V13	3.3-V LV..default		24mA
guess_segs_1[5]	Output	PIN_V14	8	B8_N0	PIN_V14	3.3-V LV..default		24mA
guess_segs_1[4]	Output	PIN_AE11	8	B8_N0	PIN_AE11	3.3-V LV..default		24mA
guess_segs_1[3]	Output	PIN_AD11	8	B8_N0	PIN_AD11	3.3-V LV..default		24mA
guess_segs_1[2]	Output	PIN_AC12	8	B8_N0	PIN_AC12	3.3-V LV..default		24mA
guess_segs_1[1]	Output	PIN_AB12	8	B8_N0	PIN_AB12	3.3-V LV..default		24mA
guess_segs_1[0]	Output	PIN_AF10	8	B8_N0	PIN_AF10	3.3-V LV..default		24mA
guess_segs_2[6]	Output	PIN_AB24	6	B6_N1	PIN_AB24	3.3-V LV..default		24mA
guess_segs_2[5]	Output	PIN_AA23	6	B6_N1	PIN_AA23	3.3-V LV..default		24mA
guess_segs_2[4]	Output	PIN_AA24	6	B6_N1	PIN_AA24	3.3-V LV..default		24mA
guess_segs_2[3]	Output	PIN_Y22	6	B6_N1	PIN_Y22	3.3-V LV..default		24mA
guess_segs_2[2]	Output	PIN_W21	6	B6_N1	PIN_W21	3.3-V LV..default		24mA
guess_segs_2[1]	Output	PIN_V21	6	B6_N1	PIN_V21	3.3-V LV..default		24mA
guess_segs_2[0]	Output	PIN_V20	6	B6_N1	PIN_V20	3.3-V LV..default		24mA
guess_segs_3[6]	Output	PIN_Y24	6	B6_N1	PIN_Y24	3.3-V LV..default		24mA
guess_segs_3[5]	Output	PIN_AB25	6	B6_N1	PIN_AB25	3.3-V LV..default		24mA
guess_segs_3[4]	Output	PIN_AB26	6	B6_N1	PIN_AB26	3.3-V LV..default		24mA
guess_segs_3[3]	Output	PIN_AC26	6	B6_N1	PIN_AC26	3.3-V LV..default		24mA
guess_segs_3[2]	Output	PIN_AC25	6	B6_N1	PIN_AC25	3.3-V LV..default		24mA
guess_segs_3[1]	Output	PIN_V22	6	B6_N1	PIN_V22	3.3-V LV..default		24mA
guess_segs_3[0]	Output	PIN_AB23	6	B6_N1	PIN_AB23	3.3-V LV..default		24mA
guess_segs_4[6]	Output	PIN_W24	6	B6_N1	PIN_W24	3.3-V LV..default		24mA
guess_segs_4[5]	Output	PIN_U22	6	B6_N1	PIN_U22	3.3-V LV..default		24mA
guess_segs_4[4]	Output	PIN_Y25	6	B6_N1	PIN_Y25	3.3-V LV..default		24mA
guess_segs_4[3]	Output	PIN_Y26	6	B6_N1	PIN_Y26	3.3-V LV..default		24mA
guess_segs_4[2]	Output	PIN_AA26	6	B6_N1	PIN_AA26	3.3-V LV..default		24mA
guess_segs_4[1]	Output	PIN_AA25	6	B6_N1	PIN_AA25	3.3-V LV..default		24mA
guess_segs_4[0]	Output	PIN_Y23	6	B6_N1	PIN_Y23	3.3-V LV..default		24mA
LF8R_generate	Input	PIN_W26	6	B6_N1	PIN_W26	3.3-V LV..default		24mA
points[3]	Output	PIN_AC22	7	B7_N0	PIN_AC22	3.3-V LV..default		24mA
points[2]	Output	PIN_AB21	7	B7_N0	PIN_AB21	3.3-V LV..default		24mA
points[1]	Output	PIN_AF23	7	B7_N0	PIN_AF23	3.3-V LV..default		24mA
points[0]	Output	PIN_AE23	7	B7_N0	PIN_AE23	3.3-V LV..default		24mA
reset	Input	PIN_N26	5	B5_N1	PIN_N26	3.3-V LV..default		24mA
rng_segs_1[6]	Output	PIN_T3	1	B1_N0	PIN_T3	3.3-V LV..default		24mA
rng_segs_1[5]	Output	PIN_R6	1	B1_N0	PIN_R6	3.3-V LV..default		24mA
rng_segs_1[4]	Output	PIN_R7	1	B1_N0	PIN_R7	3.3-V LV..default		24mA
rng_segs_1[3]	Output	PIN_T4	1	B1_N0	PIN_T4	3.3-V LV..default		24mA
rng_segs_1[2]	Output	PIN_U2	1	B1_N0	PIN_U2	3.3-V LV..default		24mA
rng_segs_1[1]	Output	PIN_U1	1	B1_N0	PIN_U1	3.3-V LV..default		24mA
rng_segs_1[0]	Output	PIN_U9	1	B1_N0	PIN_U9	3.3-V LV..default		24mA
rng_segs_2[6]	Output	PIN_R3	1	B1_N0	PIN_R3	3.3-V LV..default		24mA
rng_segs_2[5]	Output	PIN_R4	1	B1_N0	PIN_R4	3.3-V LV..default		24mA
rng_segs_2[4]	Output	PIN_R5	1	B1_N0	PIN_R5	3.3-V LV..default		24mA
rng_segs_2[3]	Output	PIN_T9	1	B1_N0	PIN_T9	3.3-V LV..default		24mA
rng_segs_2[2]	Output	PIN_P7	1	B1_N0	PIN_P7	3.3-V LV..default		24mA
rng_segs_2[1]	Output	PIN_P6	1	B1_N0	PIN_P6	3.3-V LV..default		24mA
rng_segs_2[0]	Output	PIN_T2	1	B1_N0	PIN_T2	3.3-V LV..default		24mA
rng_segs_3[6]	Output	PIN_M4	2	B2_N1	PIN_M4	3.3-V LV..default		24mA
rng_segs_3[5]	Output	PIN_M5	2	B2_N1	PIN_M5	3.3-V LV..default		24mA
rng_segs_3[4]	Output	PIN_M3	2	B2_N1	PIN_M3	3.3-V LV..default		24mA
rng_segs_3[3]	Output	PIN_M2	2	B2_N1	PIN_M2	3.3-V LV..default		24mA
rng_segs_3[2]	Output	PIN_P3	1	B1_N0	PIN_P3	3.3-V LV..default		24mA
rng_segs_3[1]	Output	PIN_P4	1	B1_N0	PIN_P4	3.3-V LV..default		24mA
rng_segs_3[0]	Output	PIN_R2	1	B1_N0	PIN_R2	3.3-V LV..default		24mA
rng_segs_4[6]	Output	PIN_N9	2	B2_N1	PIN_N9	3.3-V LV..default		24mA
rng_segs_4[5]	Output	PIN_P9	2	B2_N1	PIN_P9	3.3-V LV..default		24mA
rng_segs_4[4]	Output	PIN_L7	2	B2_N1	PIN_L7	3.3-V LV..default		24mA
rng_segs_4[3]	Output	PIN_L6	2	B2_N1	PIN_L6	3.3-V LV..default		24mA
rng_segs_4[2]	Output	PIN_L9	2	B2_N1	PIN_L9	3.3-V LV..default		24mA
rng_segs_4[1]	Output	PIN_L2	2	B2_N1	PIN_L2	3.3-V LV..default		24mA
rng_segs_4[0]	Output	PIN_L3	2	B2_N1	PIN_L3	3.3-V LV..default		24mA
points[7]	Unknown	PIN_AC21	7	B7_N0		3.3-V LV..default		24mA
points[6]	Unknown	PIN_AD21	7	B7_N0		3.3-V LV..default		24mA
points[5]	Unknown	PIN_AD23	7	B7_N0		3.3-V LV..default		24mA
points[4]	Unknown	PIN_AD22	7	B7_N0		3.3-V LV..default		24mA
<< new node >>								24mA



#### **4. Video**

Video link: <https://youtu.be/WUGZxaSniOU>

#### **5. Code**

Code link: <https://github.com/YanaiAvila/cpe-302/blob/main/CPE302-Final-Project-Code.vhd>

#### **6. Future Improvements**

One of the things I would have liked to figure out with this project is how to implement a sequence on the VGA monitor to provide a visual of the colors instead of the labels on the 7-segment displays. This was the original plan which is why I made this game to have colors. I was unable to figure out what I was doing wrong when trying to display something on the VGA monitor. Because of this, I decided to quickly re-adjust my project into a much simpler one using the 7-segments to demonstrate the concept, but adding a monitor display would not be too difficult if given more time.

Another improvement I would make is to be able to add the points for each round. The way I have it now, the player can only see their points for each round. I would like to have it so that these points accumulate and the player wins at a certain amount of points.